

## Circuits Practice

1.) Determine the equivalent (total) resistance for each of the following circuits below.

$$a.) \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \quad \frac{1}{R_p} = \frac{1}{7} + \frac{1}{5} + \frac{1}{2} \quad \frac{1}{R_p} = 1.18 \Omega$$

$$b.) R_s = R_1 + R_2 + R_3 \dots + R_n \quad R_s = 5 + 2 \quad R_s = 7 \Omega$$

$$c.) R_s = R_1 + R_2 + R_3 \dots + R_n \quad R_s = 5 + 2 + 7 \quad R_s = 14 \Omega$$


2.) Determine the total voltage (electric potential) for each of the following circuits below.

$$a.) \text{Add the voltages} = 13V$$

$$b.) \text{Add the voltages} = 12V$$


3.) Fill out the table for the circuit diagramed at the right.

<u>Circuit Position</u>	<u>Voltage (V)</u>	<u>Current (A)</u>	<u>Resistance (<math>\Omega</math>)</u>
1	1.0	0.10	10.0
2	2.0	0.10	20.0
3	3.0	0.10	30.0
Total	6.00	0.10	60.0

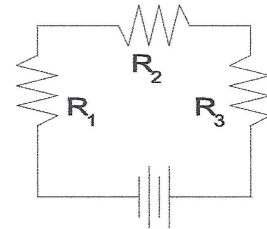


4.) Fill out the table for the circuit diagramed at the right.

<u>Circuit Position</u>	<u>Voltage (V)</u>	<u>Current (A)</u>	<u>Resistance (<math>\Omega</math>)</u>
1	6.00	0.60	10.0
2	6.00	0.30	20.0
3	6.00	0.20	30.0
Total	6.00	1.1	5.45

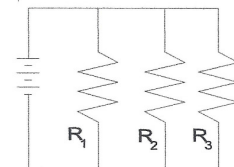


5.) Fill out the table for the circuit diagramed at the right.

<u>Circuit Position</u>	<u>Voltage (V)</u>	<u>Current (A)</u>	<u>Resistance (<math>\Omega</math>)</u>
1	2.73	0.273	10.0
2	3.27	0.164	20.0
3	3.27	0.109	30.0
Total	6.00	0.273	22.0

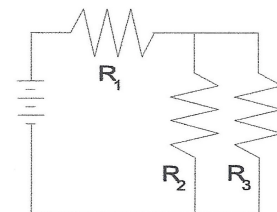

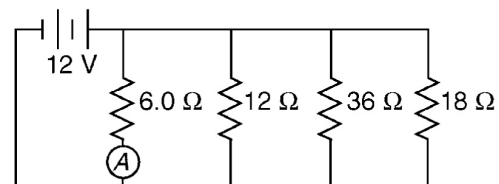Questions 6 and 7 refer to the following:





The diagram to the right represents an electric circuit consisting of four resistors and a 12-volt battery.



6.) What is the equivalent resistance of the circuit shown?  $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$   $\frac{1}{R_p} = \frac{1}{6} + \frac{1}{12} + \frac{1}{36} + \frac{1}{18}$   $\frac{1}{R_p} = 2.77 \Omega$

7.) What is the current measured by ammeter  $A$  shown in the diagram?  $V = IR$   $12 = I6.0$   $I = 2.0 A$

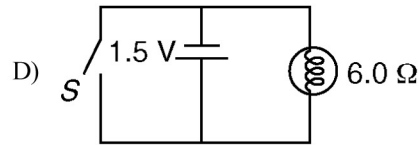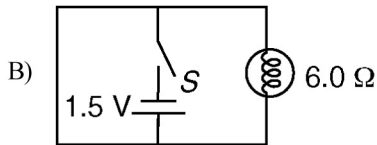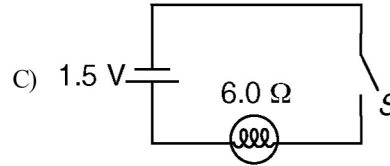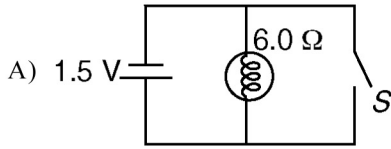
8.) A  $6.0 \Omega$  lamp requires  $0.25 A$  of current to operate. In which circuit below would the lamp operate correctly when switch  $S$  is closed?



Answer - C

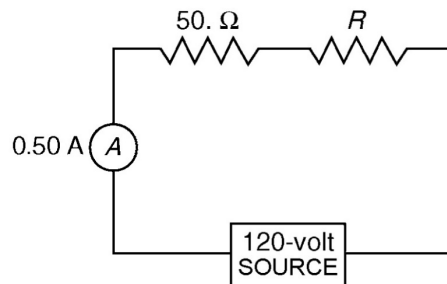Questions 9 and 10 refer to the following:

A  $50. \Omega$  resistor, an unknown resistor  $R$ , a  $120. V$  source, and an ammeter are connected in a complete circuit. The ammeter reads  $0.50 A$ .




9.) Calculate the equivalent resistance of the circuit shown.  $V = IR$   $120 = 0.50R$   $R = 240. \Omega$

10.) Determine the resistance of resistor  $R$  shown in the diagram.  $R_s = R_1 + R_2 \dots + R_n$   $240. = 50. + R$   $R_s = 190. \Omega$

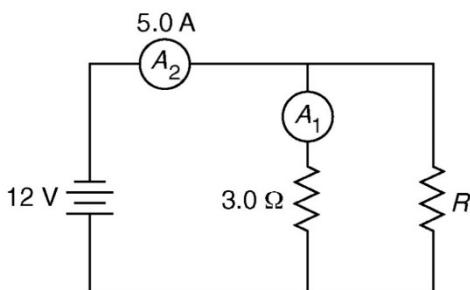Questions 11 through 13 refer to the following:

A  $3.0 \Omega$  resistor, an unknown resistor,  $R$ , and two ammeters,  $A_1$  and  $A_2$ , are connected as shown below with a  $12 V$  source. Ammeter  $A_2$  reads a current of  $5.0 A$ .



11.) Determine the equivalent resistance of the circuit shown.

$$V = IR \quad 12 = 5.0R \quad R = 2.4 \Omega$$

12.) Calculate the current measured by ammeter  $A_1$  in the diagram shown.

$$V = IR \quad 12 = I \times 3.0 \quad I = 4.0 A$$

13.) Calculate the resistance of the unknown resistor,  $R$  in the diagram shown.

$$\frac{1}{R_p} = \frac{1}{R_1} + \dots + \frac{1}{R_n} \quad \frac{1}{2.4} = \frac{1}{R} + \frac{1}{3} \quad R_p = 12 \Omega$$

14.) The load across a 50.0 V battery consists of a series combination of two lamps with resistances of 125  $\Omega$ , and 225  $\Omega$ .

a. Find the total resistance of the circuit.

$$R_s = R_1 + R_2 \dots + R_n \quad R_s = 125 + 225 \quad R_s = 350. \Omega$$

b. Find the current in the circuit.

$$V = IR \quad 50.0 = I(350) \quad I = 0.143 \text{ A}$$

c. Find the potential difference across the 125  $\Omega$  lamp.

$$V = IR \quad V = (0.143)(125) \quad I = 17.9 \text{ V}$$

15.) The load across a 12 V battery consists of a series combination of three resistances. They are 15  $\Omega$ , 21  $\Omega$ , and 24  $\Omega$ , respectively.

a. Draw the circuit diagram.

b. What is the total resistance of the load?

$$R_s = R_1 + R_2 \dots + R_n \quad R_s = 15 + 21 + 24 \quad R_s = 60. \Omega$$

c. What is the magnitude of the circuit current?

$$V = IR \quad 12 = I \times 60. \quad I = 0.20 \text{ A}$$

16.) The load across a 40 V battery consists of a series combination of three resistances  $R_1$ ,  $R_2$ , and  $R_3$ .  $R_1$  is 240.  $\Omega$  and  $R_3$  is 120.  $\Omega$ . The potential difference across  $R_1$  is 24 V.

a. Find the current in the circuit.

$$V = IR \quad 24 = I \times 240. \quad I = 0.10 \text{ A}$$

b. Find the equivalent resistance of the circuit.

$$V = IR \quad 40 = 0.10 \times R \quad R = 400 \Omega$$

c. Find the resistance of  $R_2$ .

$$R_s = R_1 + R_2 \dots + R_n \quad 400 = 240 + 120 + R_2 \quad R_2 = 40. \Omega$$

17.) The load across a 12 V battery consists of a series combination of three resistances  $R_1$ ,  $R_2$ , and  $R_3$ .  $R_1$  is 210.  $\Omega$ ,  $R_2$  is 350.  $\Omega$ , and  $R_3$  is 120.  $\Omega$ .

a. Find the equivalent resistance of the circuit.

$$R_s = R_1 + R_2 \dots + R_n \quad R_s = 210. + 350. + 120. \quad R_s = 680. \Omega$$

b. Find the current in the circuit.

$$V = IR \quad 12 = I \times 680. \quad I = 0.018 \text{ A}$$

c. Find the potential difference across  $R_3$ .

$$V = IR \quad V = 0.01764 \times 120. \quad V = 2.12 \text{ V}$$

18.) Two resistances, one 12  $\Omega$  and the other 18  $\Omega$ , are connected in parallel. What is the equivalent resistance of the parallel combination?

$$\frac{1}{R_p} = \frac{1}{R_1} + \dots + \frac{1}{R_n} \quad \frac{1}{R_p} = \frac{1}{12} + \frac{1}{18} \quad R_p = 7.2 \Omega$$

19.) Three resistances of 12  $\Omega$  each are connected in parallel. What is the equivalent resistance?

$$\frac{1}{R_p} = \frac{1}{R_1} + \dots + \frac{1}{R_n} \quad \frac{1}{R_p} = \frac{1}{12} + \frac{1}{12} + \frac{1}{12} \quad R_p = 4.0 \Omega$$

20.) Two resistances, one 62  $\Omega$  and the other 88  $\Omega$ , are connected in parallel. The resistors are then connected to a 12 V battery.

a. What is the equivalent resistance of the parallel combination?

$$\frac{1}{R_p} = \frac{1}{R_1} + \dots + \frac{1}{R_n} \quad \frac{1}{R_p} = \frac{1}{62} + \frac{1}{88} \quad R_p = 36 \Omega$$

b. What is the current through each resistor?

$$V = IR \quad 12 = (I)(62) \quad I = 0.19 \text{ A}$$

$$V = IR \quad 12 = (I)(88) \quad I = 0.14 \text{ A}$$

21.) A 110. V household circuit that contains an 1800. W microwave, a 1000. W toaster, and an 800. W coffeemaker is connected to a 20. A fuse. Determine the current. Will the fuse melt if the microwave and the coffeemaker are both on?

$$P = VI \quad 2600 = (110.)(I) \quad I = 23.6 \text{ A}$$

Yes, 20 A fuse is too small.

22.) A 35  $\Omega$ , 55  $\Omega$ , and 85  $\Omega$  resistor are connected in parallel. The resistors are then connected to a 35 V battery.

a. What is the equivalent resistance of the parallel combination?

$$\frac{1}{R_p} = \frac{1}{R_1} + \dots + \frac{1}{R_n} \quad \frac{1}{R_p} = \frac{1}{35} + \frac{1}{55} + \frac{1}{85} \quad R_p = 17 \Omega$$

b. What is the current through each resistor?

$$V = IR \quad 35 = I \times 35. \quad I = 1.0 \text{ A}$$

$$V = IR \quad 35 = I \times 55. \quad I = 0.64 \text{ A}$$

$$V = IR \quad 35 = I \times 85. \quad I = 0.41 \text{ A}$$

23.) Resistors  $R_1$ ,  $R_2$ , and  $R_3$  have resistances of 15.0  $\Omega$ , 9.0  $\Omega$ , and 8.0  $\Omega$  respectively.  $R_1$  and  $R_2$  are connected in series, and their combination is in parallel with  $R_3$  to form a load across a 6.0 V battery.

a. Draw the circuit diagram.



b. What is the total resistance of the load?

$$\frac{1}{R_p} = \frac{1}{R_1} + \dots + \frac{1}{R_n} \quad \frac{1}{R_p} = \frac{1}{24} + \frac{1}{8.0} \quad R_p = 6.0 \Omega$$

c. What is the current in  $R_3$ ?


$$V = IR \quad 6.0 = I \times 8.0. \quad I = 0.75 \text{ A}$$

d. What is the potential difference across  $R_2$ ?

$$V = IR \quad V = 0.25 \times 9.0 \quad V = 2.25 \text{ V}$$

24.) A 15.0  $\Omega$  resistor is connected in series to a 120 V generator and two 10.0  $\Omega$  resistors that are connected in parallel to each other.

a. Draw the circuit diagram.

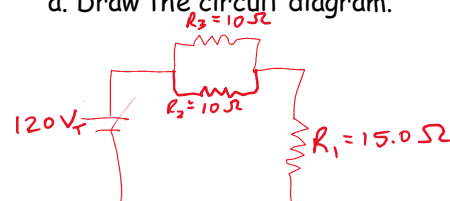

b. What is the total resistance of the load?

$$R_s = R_1 + R_2 \dots + R_n \quad R_s = 15 + 5 \quad R_s = 20. \Omega$$

c. What is the magnitude of the circuit current?

$$V = IR \quad 120 = I \times 20. \quad I = 6.0 \text{ A}$$

d. What is the current in one of the  
10.0  $\Omega$  resistors?

$$V = IR \quad 30 = I \times 10. \quad I = 3.0 \text{ A}$$

e. What is the potential difference across the  
15.0  $\Omega$  resistor?

$$V = IR \quad V = 15.0 \times 6.0 \quad V = 90.0 \text{ V}$$

### Answers

- |   |                    |                   |
|---|--------------------|-------------------|
| 1a) 1.2 $\Omega$  | 1b) 7 $\Omega$     | 1c) 14 $\Omega$   |
| 2a) 13 V  | 2b) 12 V           | 6) 3.0 $\Omega$   |
| 7) 2.0 A  | 8) C               | 9) 240. $\Omega$  |
| 10) 190 $\Omega$  | 11) 2.4 $\Omega$   | 12) 4.0 A         |
| 13) 12 $\Omega$   | 14a) 350. $\Omega$ | 14b) 0.143 A      |
| 14c) 17.9 V   | 15b) 60. $\Omega$  | 15c) 0.20 A       |
| 16a) 0.10 A   | 16b) 400. $\Omega$ | 16c) 40. $\Omega$ |
| 17a) 680. $\Omega$  | 17b) 0.018 A       | 17c) 2.1 V        |
| 18) 7.2 $\Omega$  | 19) 4.0 $\Omega$   | 20a) 36 $\Omega$  |
| 20b) 62 $\Omega = 0.19 \text{ A}$ ; 88 $\Omega = 0.14 \text{ A}$                                  |                    |                   |
| 21) $I = 23.6 \text{ A}$ so fuse will pop   | 22a) 17 $\Omega$   |                   |
| 22b) 135 $\Omega = 1.0 \text{ A}$ ; 155 $\Omega = 0.64 \text{ A}$ ; 185 $\Omega = 0.41 \text{ A}$ |                    |                   |
| 23b) 6.0 $\Omega$   | 23c) 0.75 A        | 23d) 2.3 V        |
| 24b) 20.0 $\Omega$  | 24c) 6.0 A         | 24d) 3.0 A        |
| 24e) 90. V  |                    |                   |