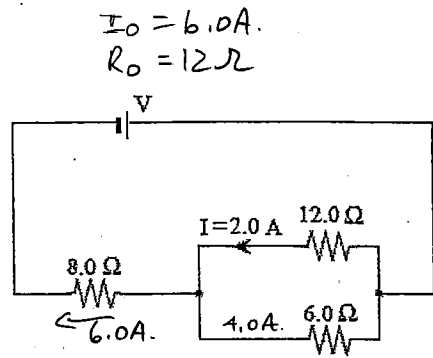


PHYSICS 11

Electric Circuits 2


1. What is the voltage, V, of the power supply shown in the circuit?

- ① Squeeze $R_p \Rightarrow \frac{1}{6} + \frac{1}{12} = \frac{1}{R_p} / R_p = 4.0 \Omega$
- ② $R_o = 8.0 \Omega + 4.0 \Omega = 12.0 \Omega$
- ③ $V_o = IR / V_o = (6.0)(12) / \boxed{V_o = 72.0 V}$



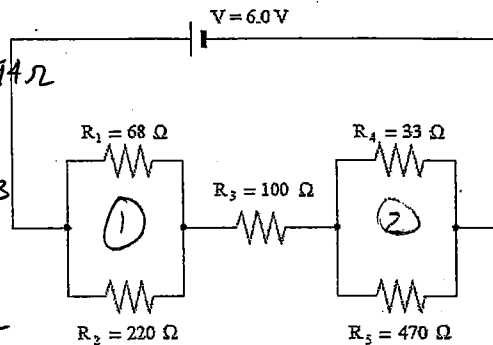
2. What is the total resistance of the circuit?

- ① $R_{p1} \Rightarrow \frac{1}{R_{p1}} = \frac{1}{68} + \frac{1}{220} / \frac{1}{R_{p1}} = \frac{288}{14960} / R_{p1} = 51.94 \Omega$
- ② $\frac{1}{R_{p2}} = \frac{1}{33} + \frac{1}{470} / \frac{1}{R_{p2}} = \frac{503}{15510} / R_{p2} = 30.83$
- ③ $R_o = 51.94 + 100 + 30.83 / \boxed{R_o = 183 \Omega}$



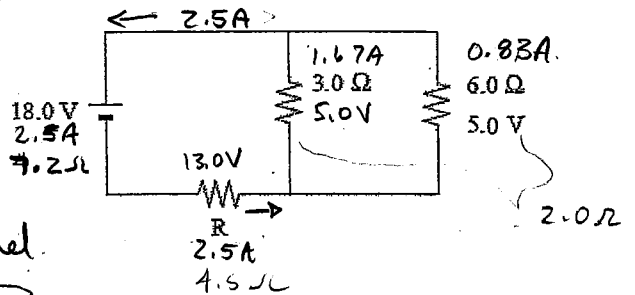
3. In the following circuit, determine the value of resistor R.

- ① Squeeze $R_p \Rightarrow \frac{1}{36} + \frac{1}{6} = \frac{1}{R_p} / R_p = 2.0 \Omega$
- ② solve V of Resistor
- ③ solve current in resistors in parallel.
- ④ $V = IR / 18.0 V = (2.5)(R) / \boxed{R_T = 7.2 \Omega}$



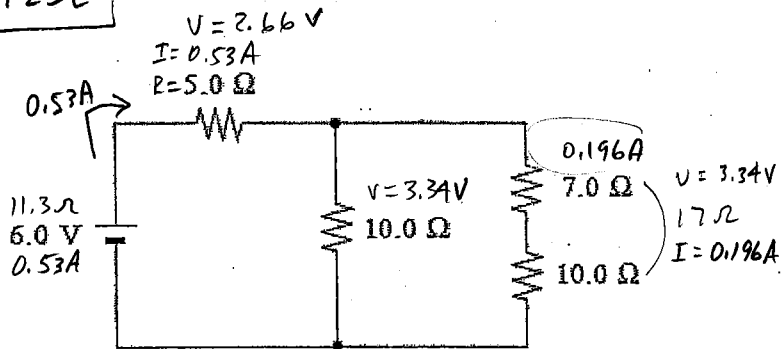4. What is the current through the 7.0 Ω resistor?
How much charge flows through the 7.0 Ω resistor in a 30 s interval?


- ① Squeeze $\rightarrow \frac{1}{R_p} = \frac{1}{10} + \frac{1}{17} / R_p = 6.296 \Omega$
- ② $R_o = 5.0 + 6.296 / R_o = 11.296 \Omega$
- ③ $V_o = IR / 6.0 = (I)(11.3) / 0.5311 A = I_o$



$I = 0.196 A / 1 Amp = \frac{C}{s} / 0.196 = \frac{Q}{30} / \boxed{5.89 \text{ Coulombs}}$

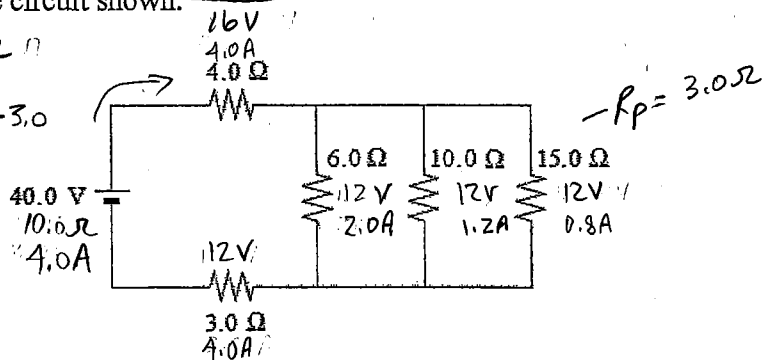5. Calculate the current through the 6.0 Ω resistor in the circuit shown.

- ① Squeeze $R_p = \frac{1}{6} + \frac{1}{10} + \frac{1}{15} / R_p = 3.0 \Omega$
- ② $R_o = R_1 + R_2 + R_3 \text{ etc.} / R_o = 4.0 + 3.0 + 3.0$
- ③ $V_o = IR / 40.0 = (I)(10) / V_o = 4.0 A$




④ $V = IR / 12 = (I)(6.0) / I = 2.0 A$

PHYSICS 11


Electric Circuits III: Power

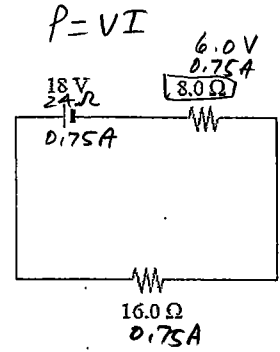1. Calculate the power dissipated by the 8.0Ω resistor in the circuit shown.

- ① $R_s = 8 + 16 / R_s = 24 \Omega$
- ② $V = IR / 18 = I(24) / I_0 = 0.75 A$
- ③ $P = (6.0)(0.75) / P = 4.5 W$




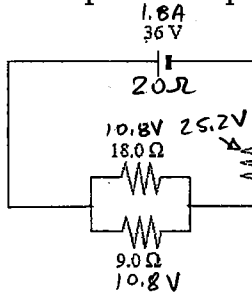2. What is the power dissipated in the 9.0Ω resistor in the following circuit?




- ① $\frac{1}{R_p} = \frac{1}{18} + \frac{1}{9} / R_p = 6 \Omega$
- ② $R_0 = 14.0 + 6.0 / R_0 = 20 \Omega$
- ③ $V_0 = IR / 36 = (I)(20) / I = 1.8 A$
- ④ $V = IR / 10.8 = (I)(9.0) / I = 1.2 A$
- ⑤ $P = VI / P = (10.8)(1.2) / P = 12.96 W$

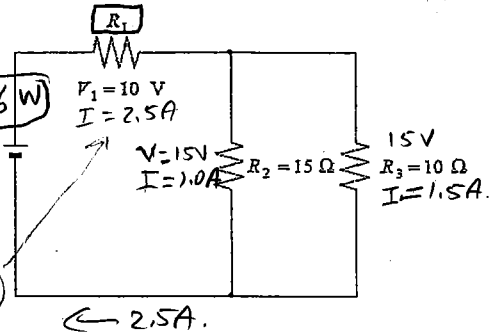3. In the following circuit, what is the power dissipated by resistor R_1 ?




- ① Solve current in both parallel resistors
 $V = IR / 15 / 15 = 1.0 A / 15 / 10 = 1.5 A$
- ② $I_0 = \text{sum of parallel currents, } 1.5 + 1.0 = 2.5 A$
- ③ $P = VI / P = (10)(2.5) / P = 25 W$

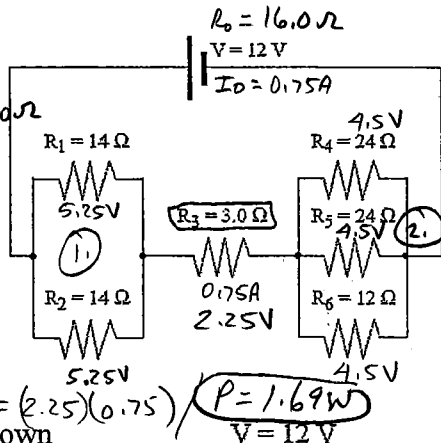4. What is the power dissipated by the 3.0Ω resistor in the circuit below?



- ① $R_p = 7.0 \Omega$
- ② $R_p \Rightarrow \frac{1}{R_p} = \frac{1}{24} + \frac{1}{24} + \frac{1}{12} / R_p = 6.0 \Omega$
- ③ $R_s = 7.0 + 6.0 + 3.0 / R_s = 16.0 \Omega$
- ④ $V_0 = IR / 12 = (I)(16) / I_0 = 0.75 A$
- ⑤ $V_1 = IR / V_1 = (0.75)(7.0) / V_1 = 5.25 V$
- ⑥ $V_2 = IR / V_2 = (0.75)(6.0) / V_2 = 4.5 V$
- ⑦ $V_3 = 12 - 4.5 - 5.25 / V_3 = 2.25 V$
- ⑧ $P = VI / P = (2.25)(0.75) / P = 1.69 W$

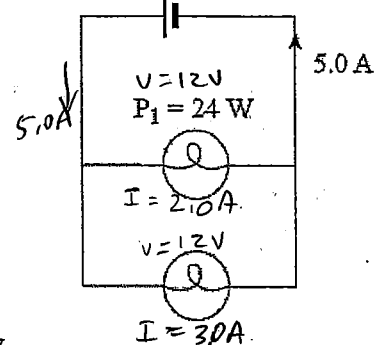5. A 12 V battery supplies a 5.0 A current to two light bulbs as shown below. The power output of one of the bulbs is $P_1 = 24 W$. What is the power output of the other bulb?



- ① $P_1 = VI / 24 = (12)(I) / I_1 = 2.0 A$
- ② $P_2 = VI / P_2 = (12)(3.0) / P_2 = 36 W$

6. A 660 W electric heater is designed to operate from a 120 V source. If the source voltage drops to 80.0 V, what will be the power dissipated by the same heater? (Assume the resistance of the heater is constant.)

$$P_1 = VI / 660 = (120)(I_1) / I_1 = 5.5 A / 120 = 5.5 (R) / R = 21.82 \Omega$$

$$V = IR / 80 = (I)(21.82) / I = 3.67 A / P = VI / P = (80)(3.67) / P = 392 W$$

7. A 75 W bulb is connected across a 120 V source. While the bulb is lighted, what is the effective resistance of the bulb?

$$P = VI / 75 = (120)(I) / I = 0.625 A / V = IR / 120 = (0.625)(R) / R = 192 \Omega$$