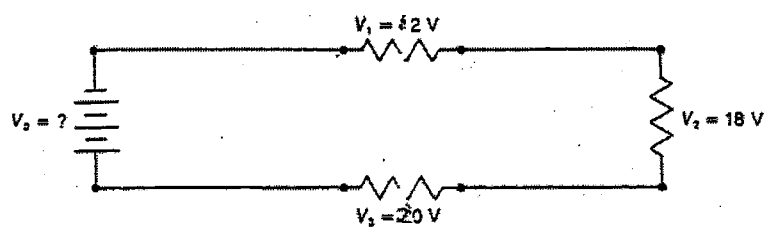


Practice - Kirchoff's Laws

Practice


1. Find V_0 in this circuit:



Loads connected in series have the same current; loads connected in parallel have the same potential difference.


$$V_T = 40V$$

2. Find I_0 in this circuit:

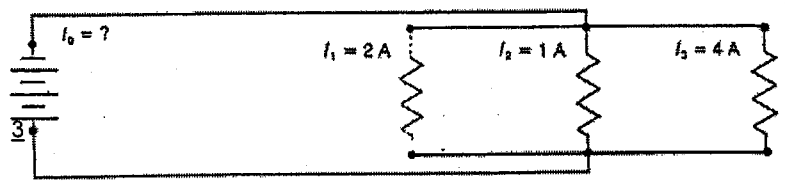

$$I_T = 7A$$

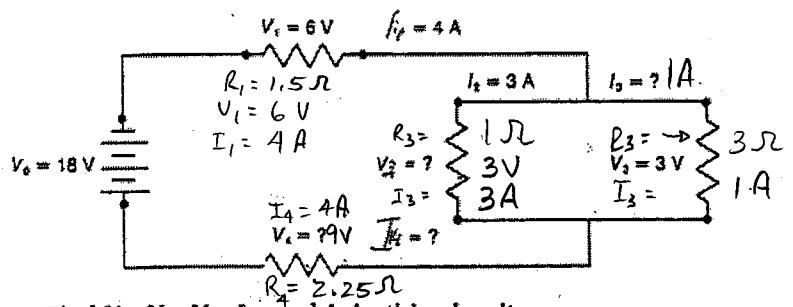3. Find V_2 , V_4 , I_3 , and I_4 in this circuit:




$$V_T = 18V$$

$$I_T = 4A$$

$$R_T = 4.5 \Omega$$

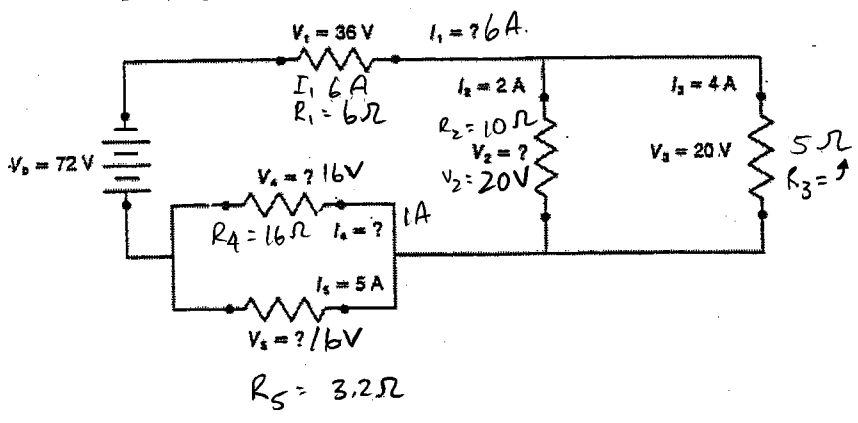4. Find V_2 , V_3 , V_4 , I_1 , and I_4 in this circuit:




$$V_T = 72V$$

$$I_T = 6A$$

$$R_T = 12 \Omega$$

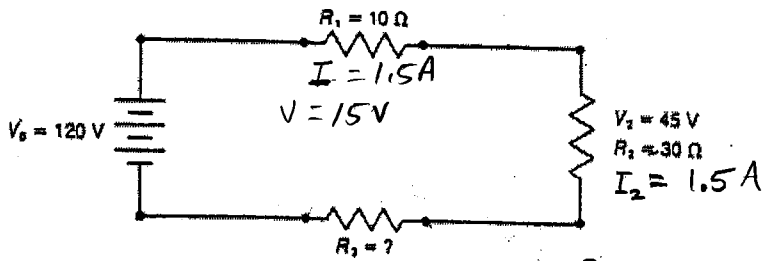
3. In this circuit, find V_1 , V_3 , I_1 , I_2 , I_3 , and R_3 .



$V_T = 120V$
 $I_T = 1.5A$
 $R_T = 80\Omega$


$I = 1.5A$ $R = 40\Omega$
 $V = 60V$

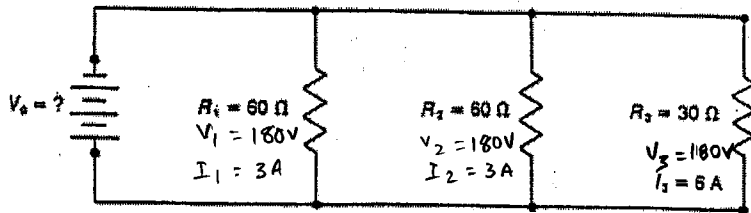4. In this circuit, find V_0 , V_1 , V_2 , V_3 , I_0 , I_1 , and I_2 .




$V_T = 180V$
 $R_T = \frac{1}{\frac{1}{60} + \frac{1}{60} + \frac{1}{30}} = \frac{1}{\frac{1}{30}} = 30\Omega$
 $I_T = 12A$

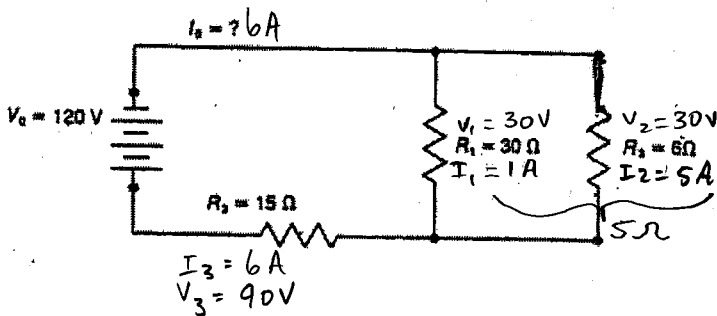5. In this circuit, find V_1 , V_2 , V_3 , I_0 , I_1 , I_2 , and I_3 .



$V_T = 120V$
 $I_T = 6A$
 $R_T = 20\Omega$

6. Solve for all.

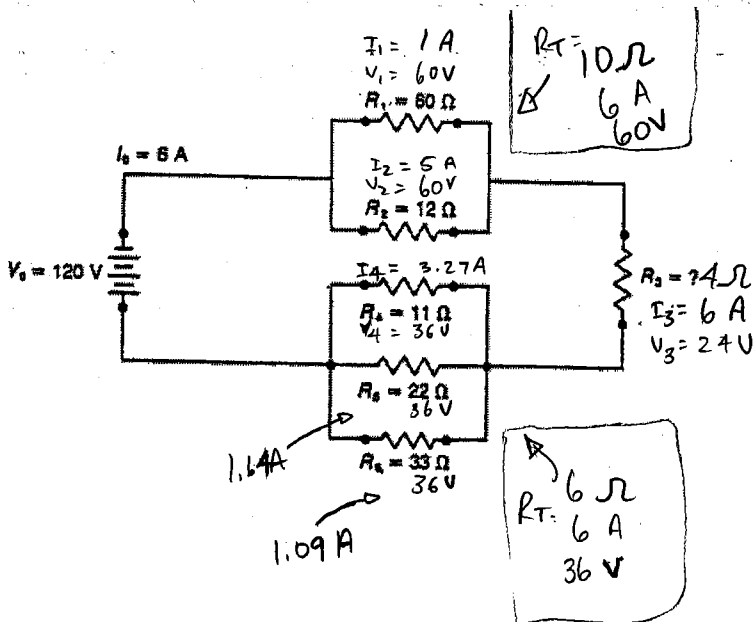

$V_T = 120V$
 $I_T = 6A$
 $R_T = 20\Omega$