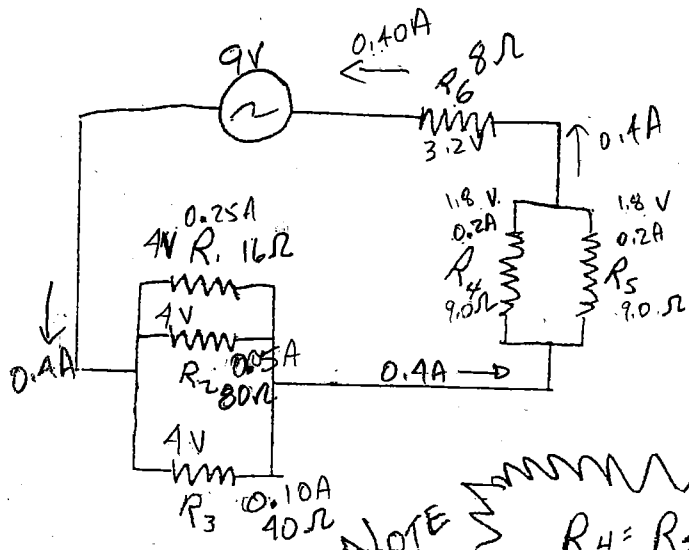


Calculate the missing values in the circuits below

1.)




$V = IR / \quad 9 = (0.4A)(R) = 22.5\Omega$

$V_0 = 9V$	$I_0 = 0.4A$
$V_1 = 4V$	$I_1 = 0.25A$
$V_2 = 4V$	$I_2 = 0.05A$
$V_3 = 4V$	$I_3 = 0.10A$
$V_4 = 0.9V$	$I_4 = 0.2A$
$V_5 = 0.9V$	$I_5 = 0.2A$
$V_6 = 3.2V$	$I_6 = 0.40A$

NOTE $R_4 = R_5$
 $R_3 = 2R_2$

2.)

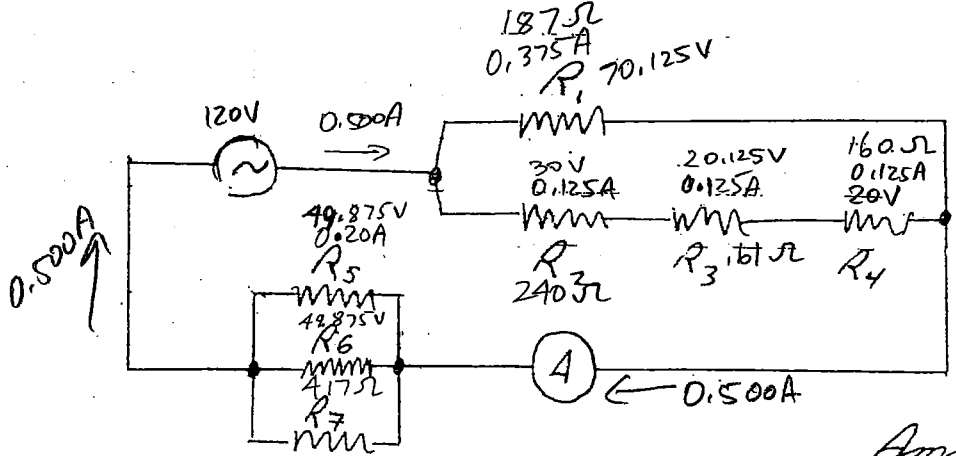


$V_0 = 120V$	$I_0 = 0.500A$	$R_0 = 240\Omega$
$V_1 = 70.125V$	$I_1 = 0.375A$	$R_1 = 187\Omega$
$V_2 = 30V$	$I_2 = 0.125A$	$R_2 = 240\Omega$
$V_3 = 20.125V$	$I_3 = 0.125A$	$R_3 = 161\Omega$
$V_4 = 20V$	$I_4 = 0.125A$	$R_4 = 160\Omega$
$V_5 = 49.875V$	$I_5 = 0.2A$	$R_5 = 249.375\Omega$
$V_6 = 49.875V$	$I_6 = 0.12A$	$R_6 = 417\Omega$
$V_7 = 49.875V$	$I_7 = 0.18$	$R_7 = 277.1\Omega$

Ammeter reads
0.500 A

$R_1, R_2, R_3, R_4 = 140.25\Omega$
 R_T
 $R_5, R_6, R_7 = 240 - 140.25 = 99.75\Omega$

NAME _____

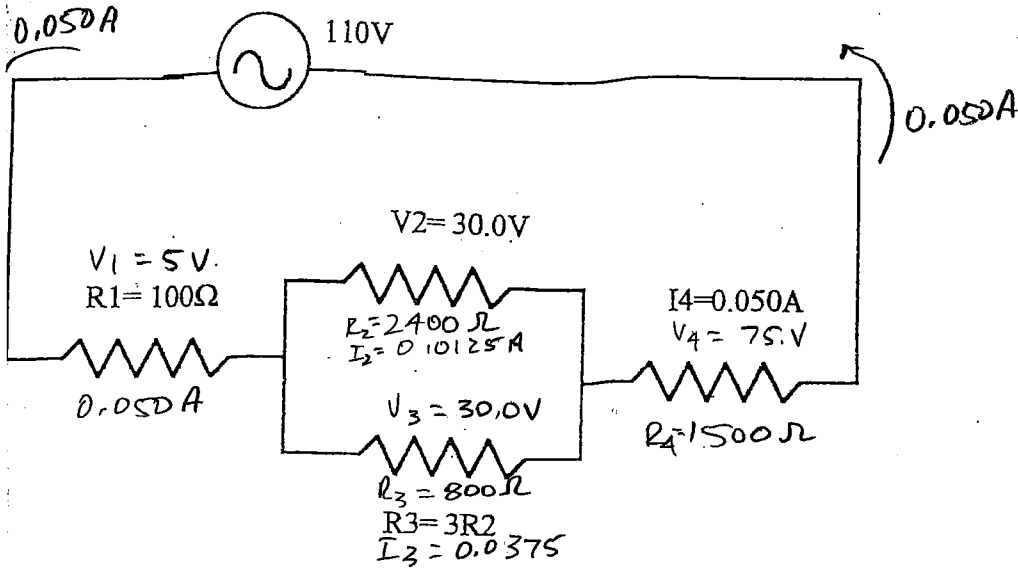Analyse the following circuits using the given information.



$$V_0 = 110V$$

$$V_1 = 5.0V$$

$$V_2 = 30.0V$$

$$V_3 = 30.0V$$

$$V_4 = 75.0V$$

$$I_0 = 0.050A$$

$$I_1 = 0.050A$$

$$I_2 = 0.0125A$$

$$I_3 = 0.0375A$$

$$I_4 = 0.050A$$

$$R_0 = 2200\Omega$$

$$R_1 = 100\Omega$$

$$R_2 = 2400\Omega$$

$$R_3 = 800\Omega$$

$$R_4 = 1500\Omega$$

$$R_2 + R_3 = 600\Omega$$

$$\frac{1}{600} = \frac{1}{R_3} + \frac{1}{3 \cdot R_2}$$

$$\frac{1}{600} = \frac{3}{3R_3} + \frac{1}{3R_2}$$

$$3 \times \frac{1}{600} = \frac{4}{3R_3}$$

$$\frac{3}{600} = \frac{4}{R_3} \quad \left| \quad \frac{600}{3} = \frac{R_3}{4} \right.$$

$$\frac{2400}{3} = R_3 \quad \left| \quad R_3 = 800 \right.$$